

EE341: Project 4

Timothy Kopp & Mark McCurry

November 30, 2010

1 Problem 6.147

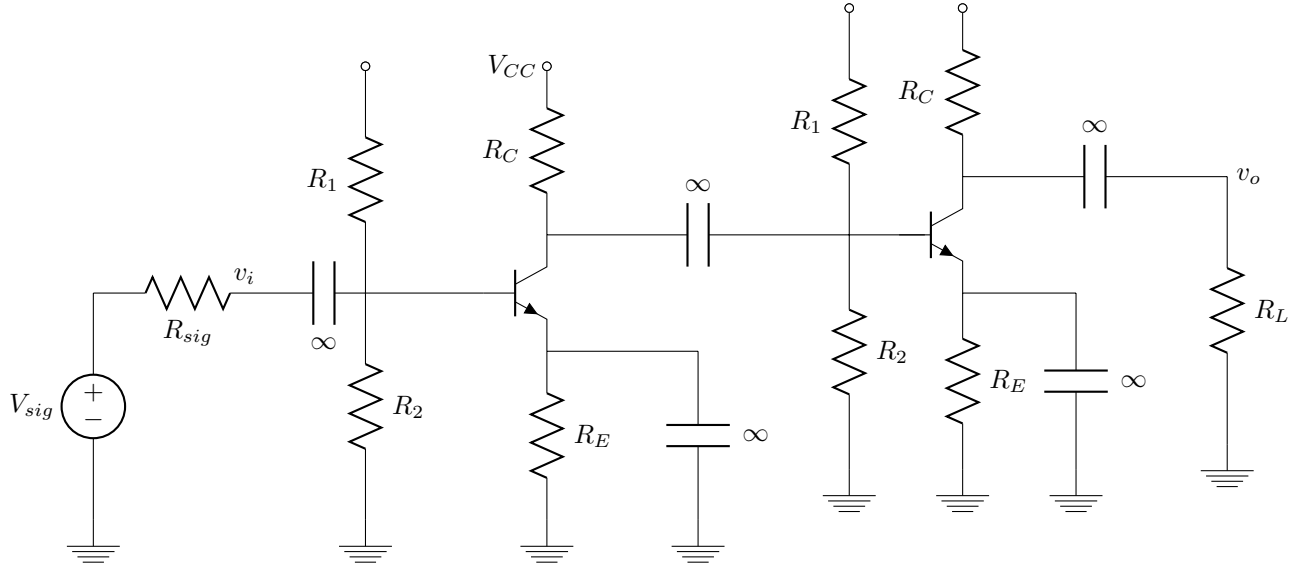


Figure 1: Large Signal Model

The problem is given as two of the amplifiers shown in Fig 1 connected with a load resistance R_L . The problem states $V_{CC} = 9V$, $R_1 = 100k\Omega$, $R_2 = 47k\Omega$, $R_E = 3.9k\Omega$, $R_C = 6.8k\Omega$, $\beta = 100$, $R_{sig} = 5k\Omega$, and $R_L = 2k\Omega$.

1.1 Hand Calculations

DC Bias: Part *a* asks for the DC collector current I_C and the DC collector voltage V_C of both transistors. For the first transistor, we replace R_1 and R_2 with their Thevinin equivalent resistance, $R_B = R_1 || R_2 = 32k\Omega$, and voltage $V_B = \frac{R_2}{R_1 + R_2} V_{BB} = 2.88V$. We then write the KVL using the large signal model, solve for I_B , and use β to find I_C .

$$V_{BB} = R_{B1} I_{B1} + 0.7V + R_{E1} I_{B1} (\beta + 1) \quad (1)$$

$$I_{B1} = 5.12\mu A \quad I_{C1} = \beta I_{B1} \quad (2)$$

$$I_{C1} = 512\mu A \quad (3)$$

We then find V_{C_1} as follows. $V_{C_1} = V_{CC} - R_{C_1}I_{C_1} = 5.5V$. For the second transistor, we observe that the connecting signal is shunted out with a large capacitance. Since the second transistor has the same parameters and associated resistances and voltages as the first, we can conclude that $I_{C_1} = I_{C_2}$ and $V_{C_1} = V_{C_2}$.

 


Figure 2: Small Signal Model

Small Signal Equivalent Circuit: Part *b* asks for the small signal equivalent circuit. Fig. 2 shows the small signal model for the entire circuit. R_{sig} is given as $5k\Omega$, R_C as $6.8k\Omega$, R_L as $2k\Omega$. R_1 and R_2 are given, so $R_1||R_2$ is calculated as $32k\Omega$. $r_e = \frac{V_T\alpha}{I_C} = 48\Omega$.

Input Resistances & Gains: Part *c* asks for the input resistance R_{in_1} and gain $\frac{v_{b_1}}{v_{sig}}$. R_{in_1} is the input resistance to the first stage, not including the signal resistance R_{sig} . The input resistance is calculated as follows.

$$R_{in_1} = (R_1||R_2)||((\beta + 1)r_e) \quad (4)$$

$$R_{in_1} = 4.24k\Omega \quad (5)$$

The gain for the first stage can be calculated as follows using R_{in_1} .

$$\frac{v_{b_1}}{v_{sig}} = \frac{R_{in_1}}{R_{sig} + R_{in_1}} \quad (6)$$

$$\frac{v_{b_1}}{v_{sig}} = 459 \frac{mV}{V} \quad (7)$$

 


Figure 3: Model

Part *d* asks for the input resistance R_{in_2} and gain from transistor one $\frac{v_{b_2}}{v_{b_1}}$. By inspection it is clear that $R_{in_2} = R_{in_1} = 4.24k\Omega$. To calculate the gain, the transistor model shown in Fig. 3 was used. To complete

the model, g_m is calculated. $g_m = \frac{\alpha}{r_e} = 20.6 \frac{mA}{V}$. R_o is simply R_C , as R_{in} of the following stage is not included. It is then simple to calculate the gain as $\frac{v_{b2}}{v_{b1}} = -g_m(R_{in2} || R_{out1}) = -51.9 \frac{V}{V}$.

Part *e* asks for the gain $\frac{v_o}{v_{b2}}$. Using the model in Fig. 3, we find that $\frac{v_o}{v_i} = g_m(R_{out2} || R_L) = -31.8 \frac{V}{V}$.

Part *f* asks for the total gain $\frac{v_o}{v_{sig}}$. This value is calculated by simply multiplying the gains from parts *c*, *d*, and *e*. We find that $\frac{v_o}{v_{sig}} = 758 \frac{V}{V}$.

1.2 Spice Verification

DC Bias: It was observed that with the used model, spice produced a V_{BE} of $756.2mV$. This was a source of error for the theoretical calculations, which were based off the assumed V_{BE} of $0.7V$.

With this value across the transistor's pins, $V_C = 5.611V$ and $I_C = 498.38\mu A$. This was the same as theoretical calculations when the different V_{BE} was accounted for.

 


Figure 4: Input to First Stage with $v_{sig} = 100\mu V$

Input & Output Resistances: R_{in} was found to be $4.2k\Omega$, where the input voltage halved in spice, as shown in Fig. 4. R_{out} was found to be $6.8k\Omega$, where the input voltage halved in spice, as shown in Fig. 5.

 


Figure 5: Output

Gains: The gains and the errors are shown in the below table. The low error indicates that a proper analysis was made.

Table 1: Gain and Error From Spice		
Name	Value	Error
Input Loss	472mV/V	2.75%
First Stage	-52.67V/V	1.46%
Second Stage	-29.15V/V	9.09%
Overall Gain	786.46V/V	3.618%

2 SPICE Source Code Listings

Listing 1: Verification of Amplifier

```
* 2 Stage Common Emitter Amplifier

*Input
vcc 10 0 DC 9
vsig 1 0 AC SIN(0 100u 10k 0 0 0)
rsig 1 2 5k

ca 2 3 100u

*First Stage
r1a 10 3 100k
r2a 3 0 47k
```

```

Qa  4  3  5  ntran
rea  5  0  3.9k
cea  5  0  100u
rca  4  10 6.8k

cb   4  6  100u

*Second stage
r1b  10 6  100k
r2b  6  0  47k
Qb   7  6  8  ntran
reb  8  0  3.9k
ceb  8  0  100u
rcb  7  10 6.8k

cc   7  9  100u

*Load
r1   9  0  2k

.model ntran npn (bf=100)

```